
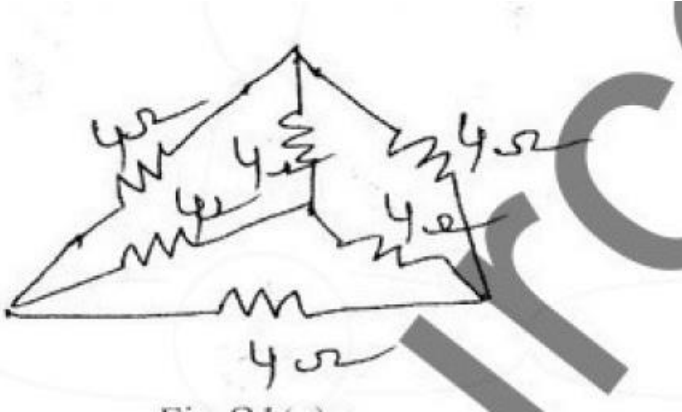
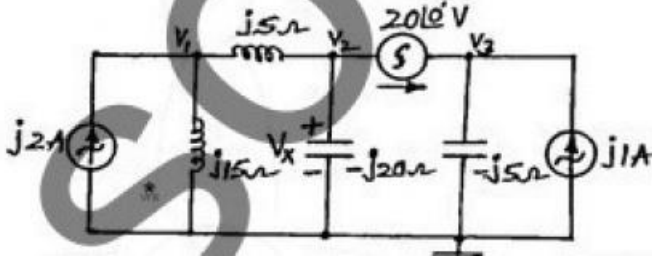
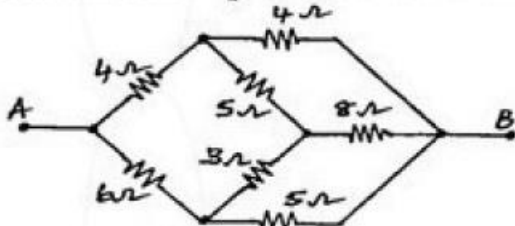
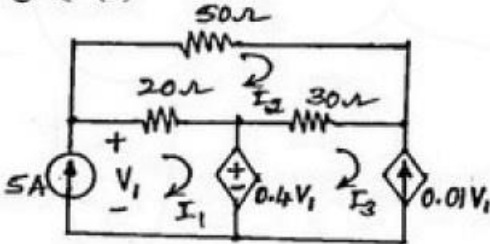


Assignment 1

1	Explain classification of electrical networks	
2	Three resistances are connected in delta obtain the star equivalent of the circuit	
3	Obtain the equivalent resistance between any two points	
4	Use the Nodal analysis and find V_x	
5	Define and explain Super mesh	
6	Use Star Delta Transformation to obtain equivalent Circuit	
7	Define Controlled sources and mention its types and applications	
8	Find V_1	


9

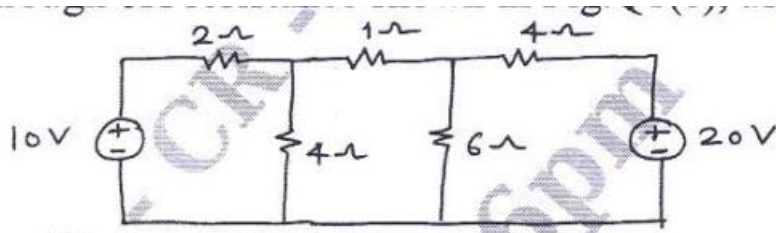Determine the current through 6 Ohm Resistor




10

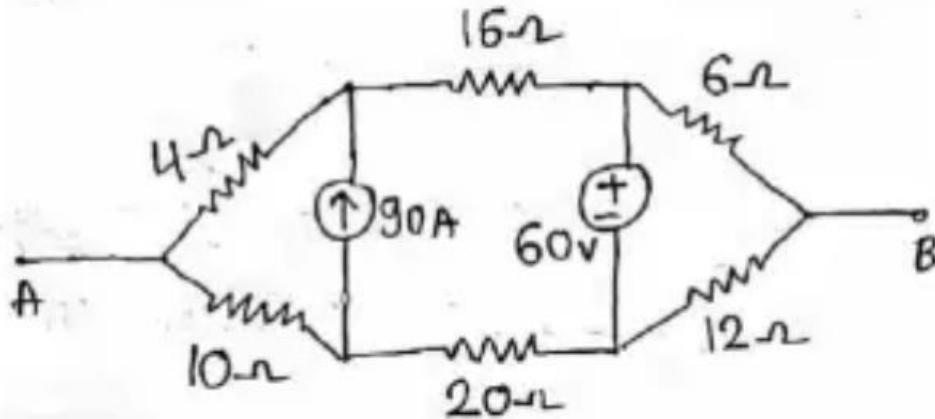Reduce the network using Source shifting and source Transformation



11

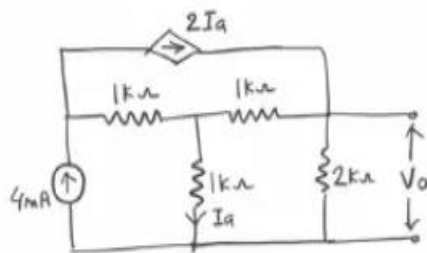Determine V_o using Mesh analysis

12

Obtain the delta connected equivalent network for the network shown in Fig.1.41 (Bangalore University)

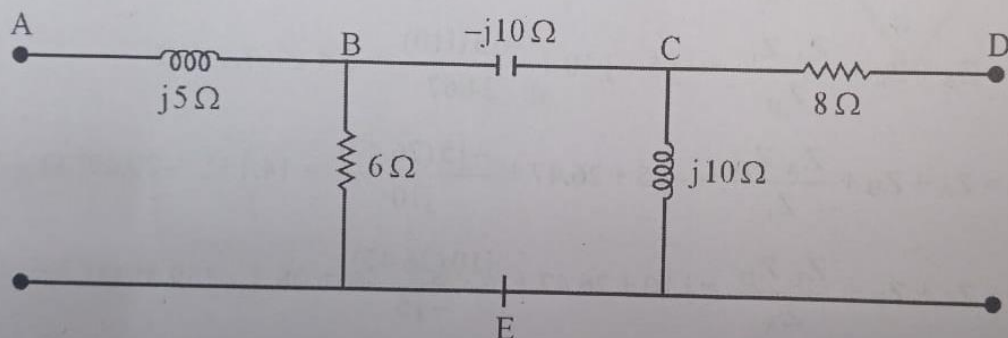
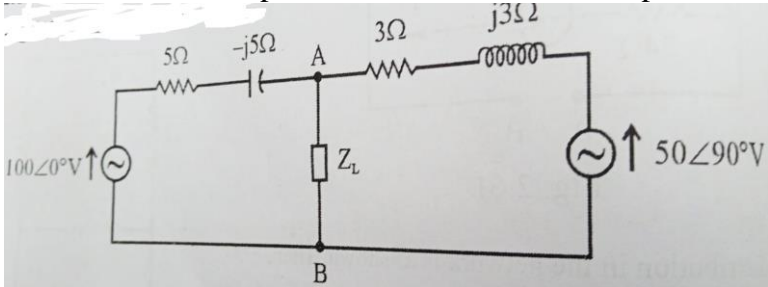
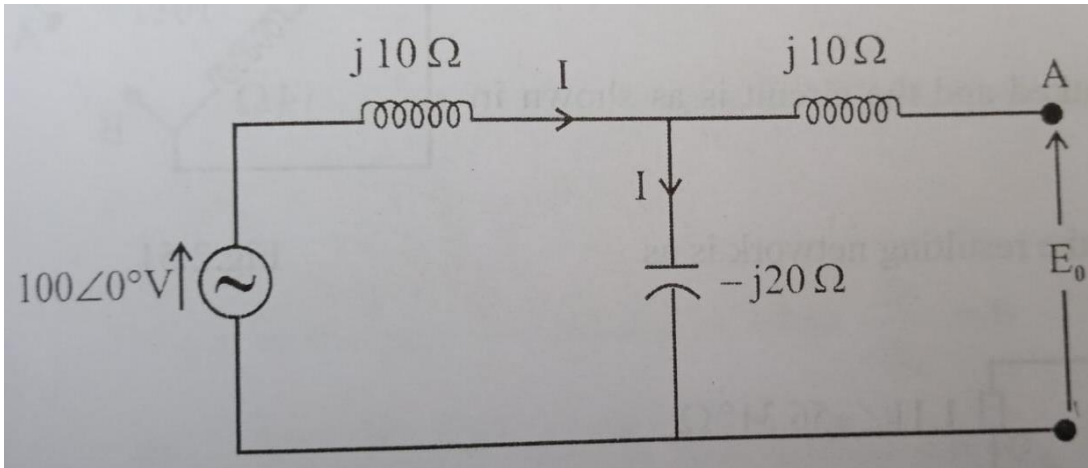


Fig. 1.41

13	<p>Explain the following Theorems</p> <ol style="list-style-type: none"> 1. Thevenins Theorem 2. Superposition Theorem 3. Nortons Theorem 4. Maximum Power Transfer Theorem including all the 3 conditions 	
14	<p>Find the Maximum power Transfer to the load impedance Z_L</p> 	
15	<p>Obtain Nortons and Thevenins Equivalent Circuit across AB.</p> 	
16	<p>Find the Nortons and Thevenins Theroem across AB</p> 